

Combinational Logic III

Logic Structures

Multiplexors

2 -1 Multiplexor

Multiplexors are used to select one of many inputs.

The _____ determines which output to select.

Draw the symbol for a 2-1 multiplexor	Finish the simplified truth table <table border="1" style="width: 100%; border-collapse: collapse; margin-top: 5px;"> <tr> <th style="width: 50%; padding: 5px;">S</th> <th style="width: 50%; padding: 5px;">Out</th> </tr> <tr> <td style="padding: 5px;">0</td> <td style="padding: 5px;"></td> </tr> <tr> <td style="padding: 5px;">1</td> <td style="padding: 5px;"></td> </tr> </table>	S	Out	0		1	
S	Out						
0							
1							
Draw the logic diagram for a 2-1 multiplexor							

4-1 Multiplexor

A 4-1 multiplexor has _____ inputs, so there are _____ select lines.

Draw the symbol for a 4-1 multiplexor	Finish the simplified truth table <table border="1" style="width: 100%; border-collapse: collapse; margin-top: 5px;"> <tr> <th style="width: 33%; padding: 5px;"></th> <th style="width: 33%; padding: 5px;"></th> <th style="width: 33%; padding: 5px;">Out</th> </tr> <tr><td style="padding: 5px;"></td><td style="padding: 5px;"></td><td style="padding: 5px;"></td></tr> <tr><td style="padding: 5px;"></td><td style="padding: 5px;"></td><td style="padding: 5px;"></td></tr> <tr><td style="padding: 5px;"></td><td style="padding: 5px;"></td><td style="padding: 5px;"></td></tr> <tr><td style="padding: 5px;"></td><td style="padding: 5px;"></td><td style="padding: 5px;"></td></tr> </table>			Out												
		Out														

Draw a logic diagram for a 4-1 multiplexor

Decoder

inputs: _____ # outputs: _____

Example: 1-2 Decoder

Draw a 1-2 decoder

Complete the truth table

in	out_1	out_0

Example: 2-4 Decoder

Draw a 2-4 decoder

Complete the truth table

in_1	in_0	out_3	out_2	out_1	out_0

Full Adder

3 inputs: _____

2 outputs: _____

Draw the schematic here:

Complete the truth table:

	A	B		

Generate the product of sums solutions for the outputs.

Four-Bit Ripple Carry Adder

Draw the schematic for a 4-bit ripple carry adder:

Draw this adder as a black box

Draw this adder as an ALU