

# Boolean Algebra

## Logic Gate Review

Draw:								
A	B	NOT A	A AND B	A NAND B	A OR B	A NOR B	A XOR B	A XNOR B

## Logical Equivalence

If the truth table for two circuits are the same, they are \_\_\_\_\_.

## Boolean Identities and Laws

Logical Inverse	$0' =$	$1' =$
Involution Law	$A'' =$	
Dominance	$A + 1 =$	$A \cdot 0 =$
Identity	$A + 0 =$	$A \cdot 1 =$

Idempotent Law	$A + A =$	$A \cdot A =$
Law of Complementarity	$A + A' =$	$A \cdot A' =$
Commutative Law	$A + B = B + A$	$A \cdot B = B \cdot A$
Associative Law	$(A + B) + C = A + (B + C)$	$(A \cdot B) \cdot C = A \cdot (B \cdot C)$
Distributive Law	$A + (B \cdot C) = (A + B) \cdot (A + C)$	$A \cdot (B + C) = (A \cdot B) + (A \cdot C)$
Absorption	$A + (AB) = A$	$A (A + B) = A$
De Morgan's Law	$A + B = (A' \cdot B')'$	$A \cdot B = (A' + B')'$

*De Morgan's Law*






1) \_\_\_\_\_ the inputs, 2) \_\_\_\_\_, 3) \_\_\_\_\_ the output

"Break the \_\_\_\_\_, change the \_\_\_\_\_"

$$A + B = (A' \cdot B')'$$

A + B			(A' · B')'					
A	B	A + B	A	B	A'	B'	A' · B'	(A' · B')'
0	0		0	0				
0	1		0	1				
1	0		1	0				
1	1		1	1				






Do the truth tables match?

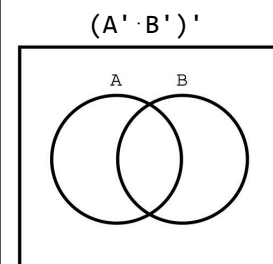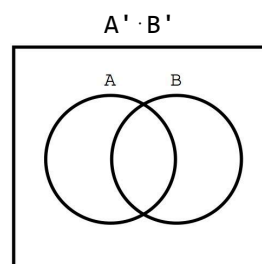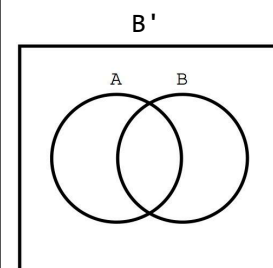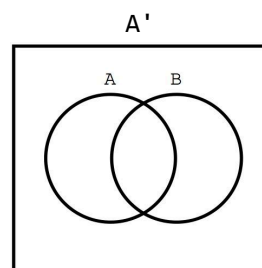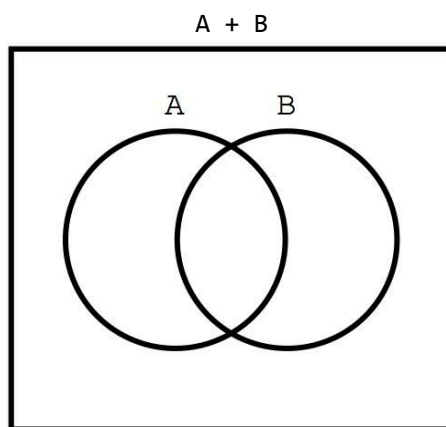

$$A \cdot B = (A' + B')'$$

$A \cdot B$			$(A' + B')'$					
A	B	$A \cdot B$	A	B	A'	B'	$A' + B'$	$(A' + B')'$
0	0		0	0				
0	1		0	1				
1	0		1	0				
1	1		1	1				

Do the truth tables match?

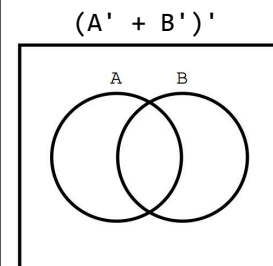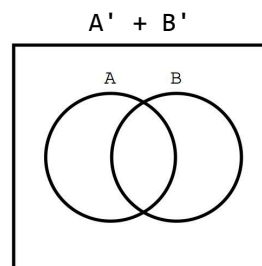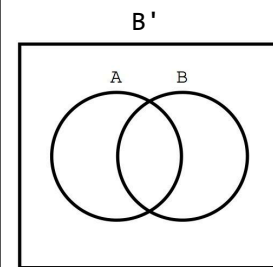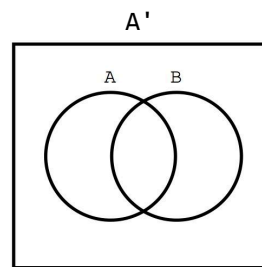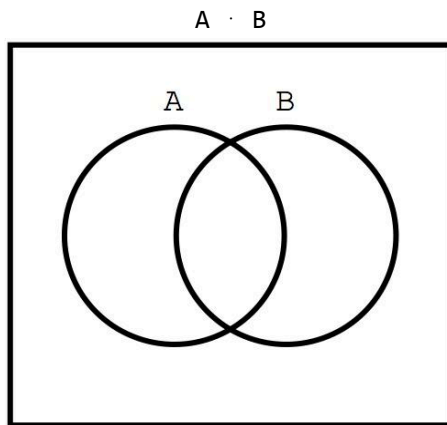



### Example

Show how  $(A \cdot B')' = A' + B$

$$A \cdot B \cdot C = (A' + B' + C')'$$

$A \cdot B \cdot C$					$(A' + B' + C')'$							
A	B	C	$A \cdot B$	$A \cdot B \cdot C$	A	B	C	A'	B'	C'	$A' + B' + C'$	$(A' + B' + C')'$
0	0	0			0	0	0					
0	0	1			0	0	1					
0	1	0			0	1	0					
0	1	1			0	1	1					
1	0	0			1	0	0					
1	0	1			1	0	1					
1	1	0			1	1	0					
1	1	1			1	1	1					

Do the truth tables match?

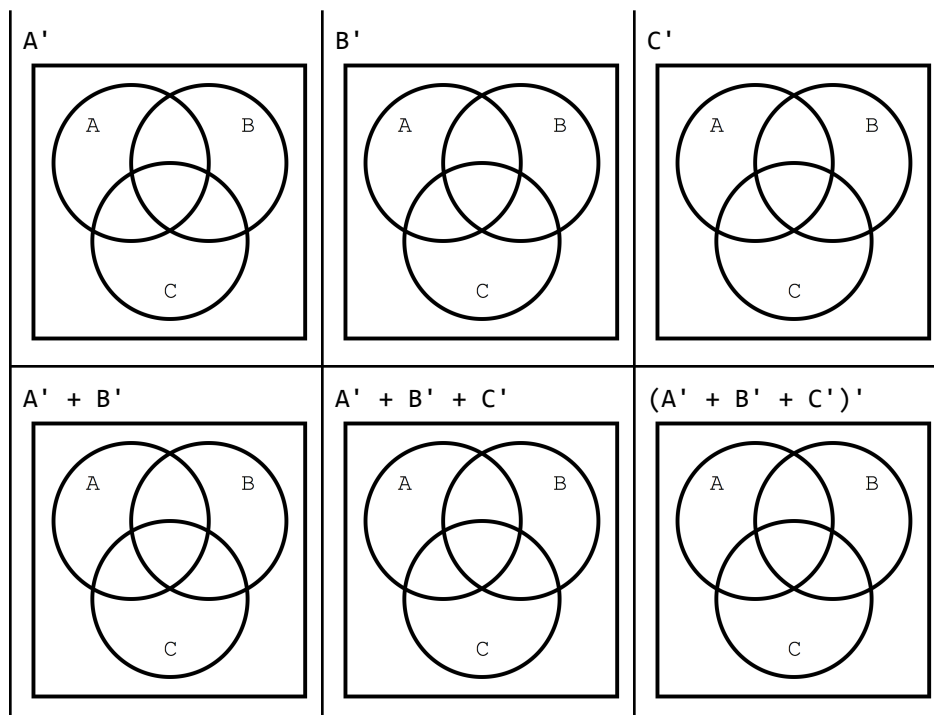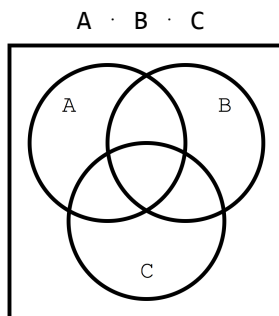

## Logical Completeness

You can create a circuit for ANY truth table with only \_\_\_\_\_

In addition, you can complete any truth table with only \_\_\_\_\_

You can also complete any truth table with only \_\_\_\_\_

### Only NANDS

Finish the truth table for  $(A \cdot B)'$ . What happens if both inputs are the same?

A	B	$(A \cdot B)'$
0	0	
0	1	
1	0	
1	1	

Draw a NOT gate using only NAND gates

Draw an AND gate using only NAND gates

Draw an OR gate using only NAND gates (hint: use DeMorgan's Law)

Draw a NOR gate using only NAND gates (hint: use DeMorgan's Law)

*Only NORs*

Finish the truth table for  $(A + B)'$ . What happens if both inputs are the same?

A	B	$(A + B)'$
0	0	
0	1	
1	0	
1	1	

Draw a NOT gate using only NOR gates

Draw an OR gate using only NOR gates

Draw an AND gate using only NOR gates (hint: use DeMorgan's Law)

Draw a NAND gate using only NOR gates (hint: use DeMorgan's Law)

### XOR Example

#### NAND Implementation

Use DeMorgan's Law to construct an XOR gate out of only NAND gates

Draw an XOR gate and complete the truth table. Generate the SOP equation.

Draw the SOP logic circuit.

Use DeMorgan's Law to convert the OR gate to an AND gate.

Combine the inverter and AND gates to form NAND gates

Convert the inverters on the inputs to NAND gates



## NOR Implementation

Use DeMorgan's Law to construct an XOR gate out of only NOR gates

Draw an XOR gate and complete the truth table. Generate the POS equation.

Draw the POS logic circuit.

Use DeMorgan's Law to convert the AND gate to an OR gate.

Combine the inverters and OR gates to form NOR gates

Convert the inverters on the inputs to NOR gates

## Logical Equivalence

If the truth table for two circuits are the same, they are logically equivalent.

Are these circuit diagrams logically equal?

Are these circuit diagrams logically equal?

Are these circuit diagrams logically equal?

Are these circuit diagrams logically equal?